

Electronics and Electricity Basics

John R. Leeman
GEARS 2023

A Few Safety Notes




- Never work on high voltage DC or any AC systems unless qualified
- This class doesn't qualify you
- Don't work on live systems if possible
- Don't work alone
- Unsure? Stop
- Did I mention this course doesn't make you an electrician?


“Anything can be a fuse” - A Mechanical Engineer



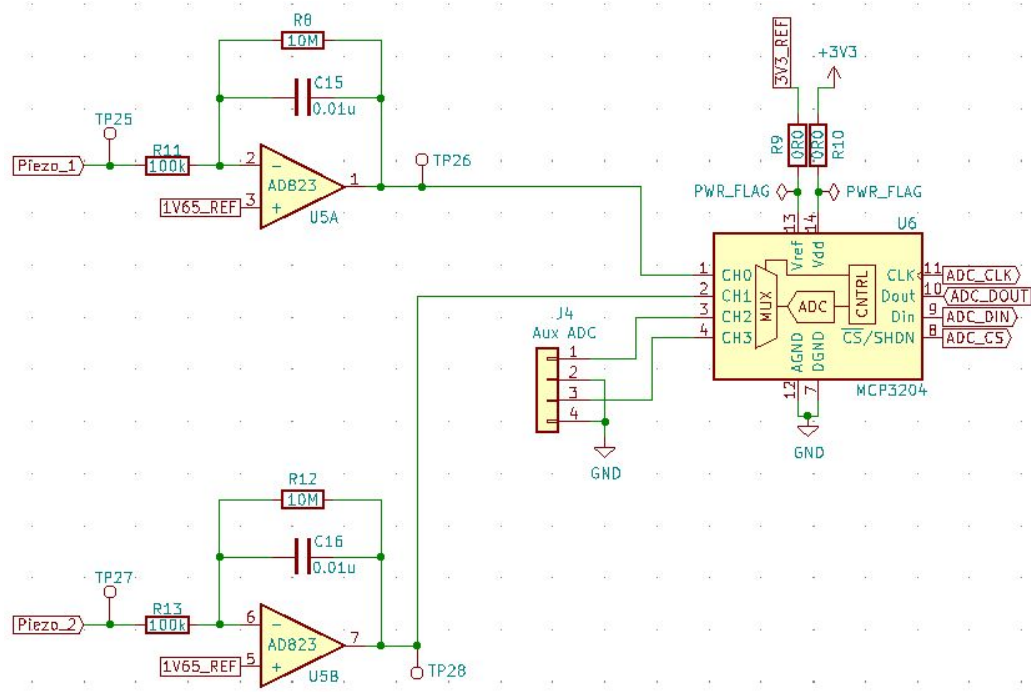
We draw circuits in schematic diagrams with symbols to represent parts and connections



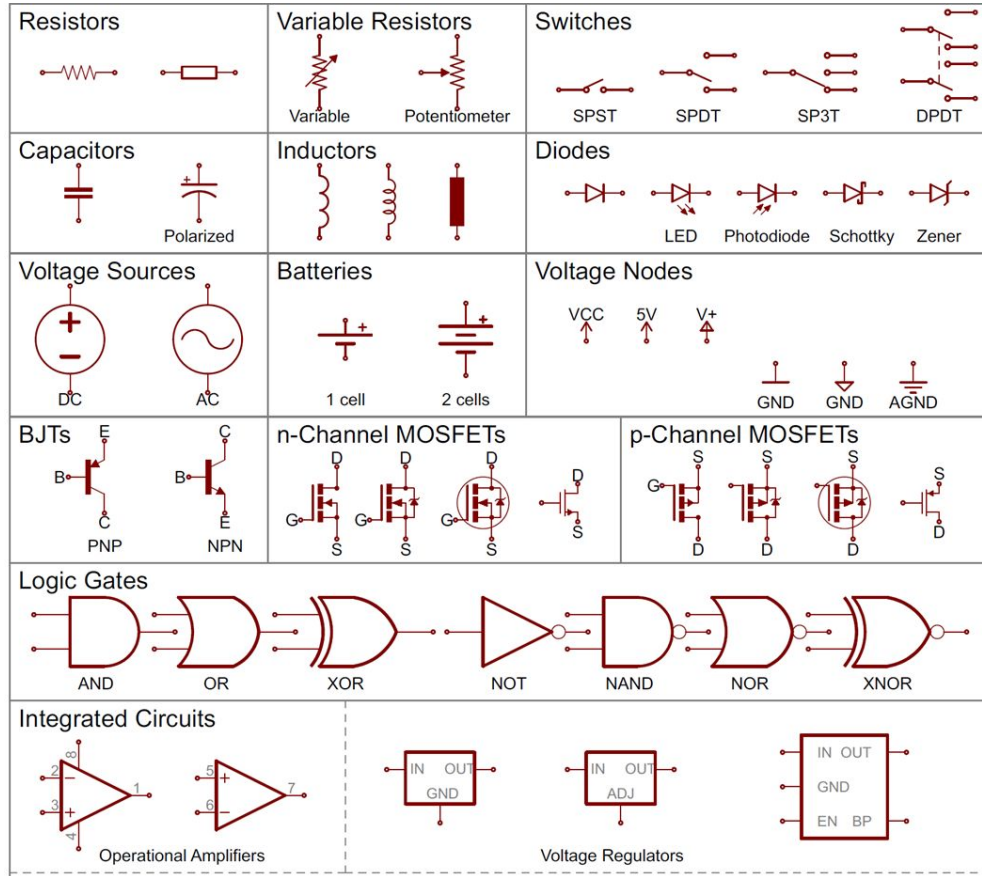
The symbols are “standard” for many components



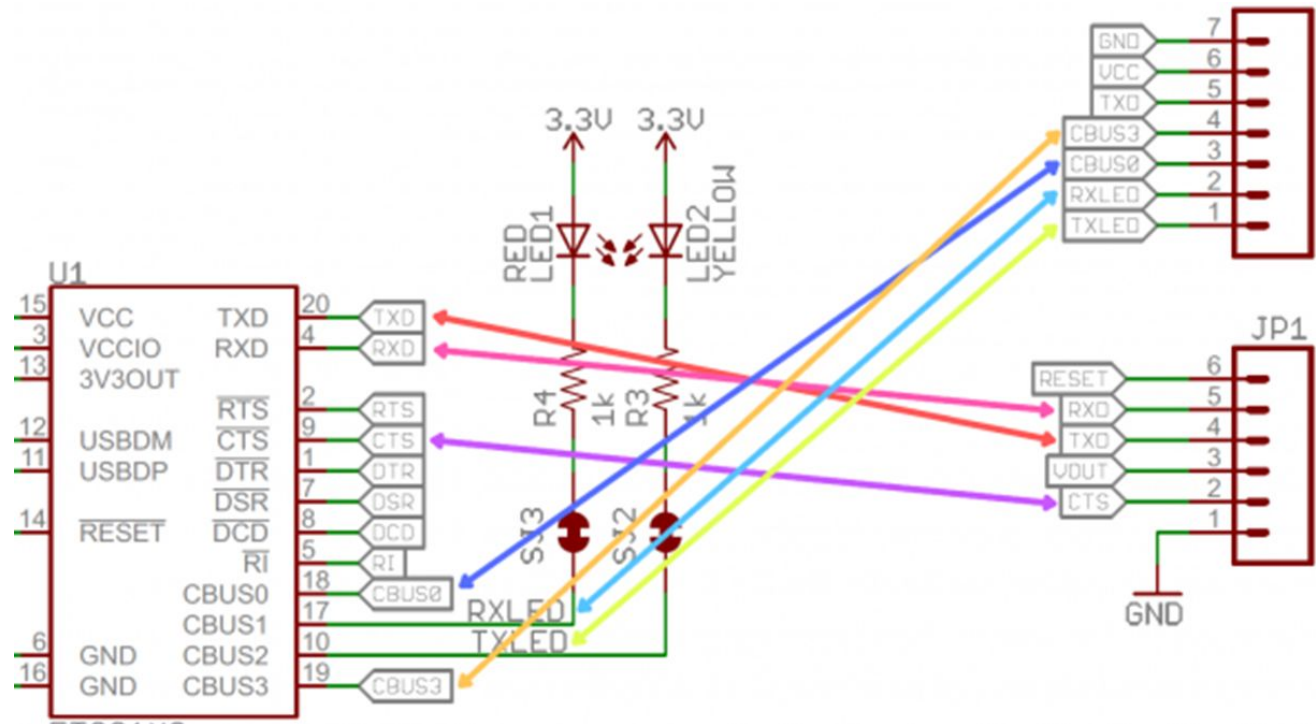We also use net name labels to reduce schematic clutter



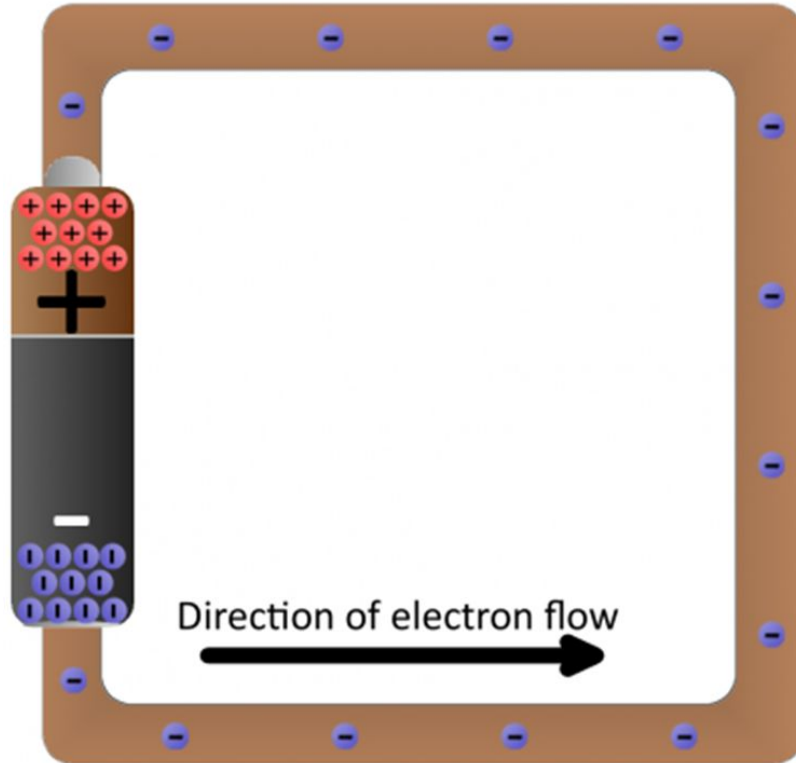Electric circuits are closed loops that electrons flow through. Electrical energy is stored electrical potential difference.





We generally think in conventional current flow, not electron flow






WE WERE GOING TO USE THE TIME MACHINE TO PREVENT THE ROBOT APOCALYPSE, BUT THE GUY WHO BUILT IT WAS AN ELECTRICAL ENGINEER.

In electronics we generally only have to consider a few fundamental quantities

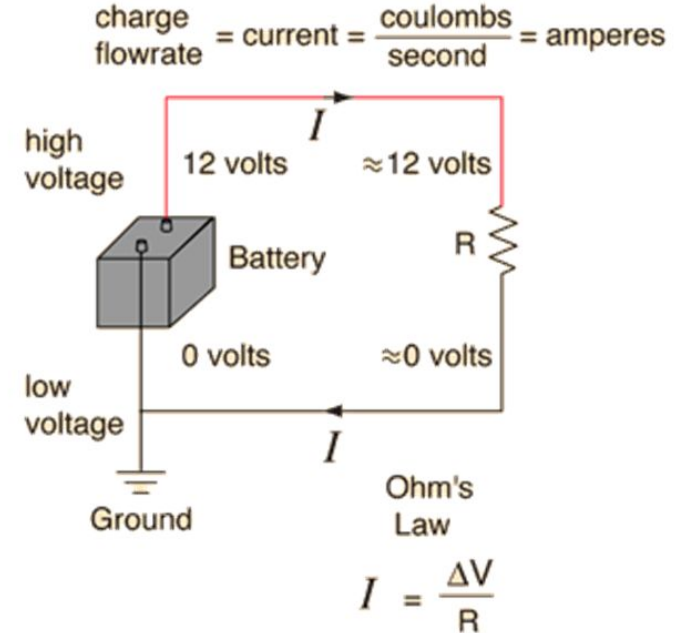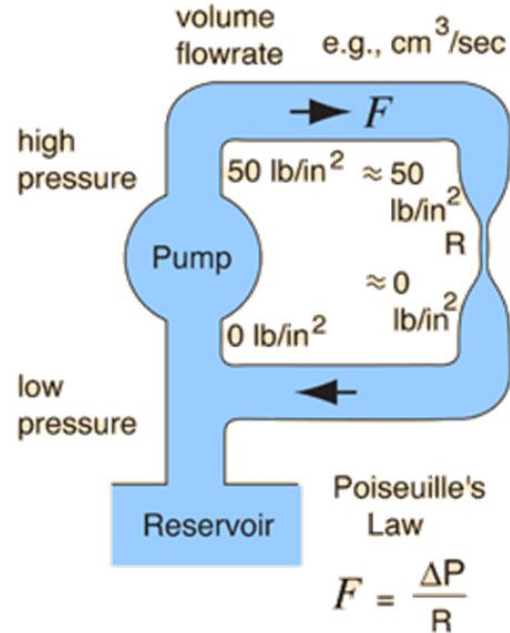
- Voltage
- Current
- Resistance
- Capacitance
- Inductance
- Reactance



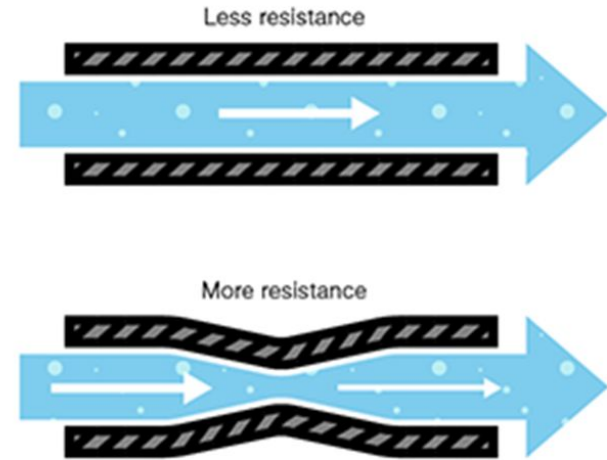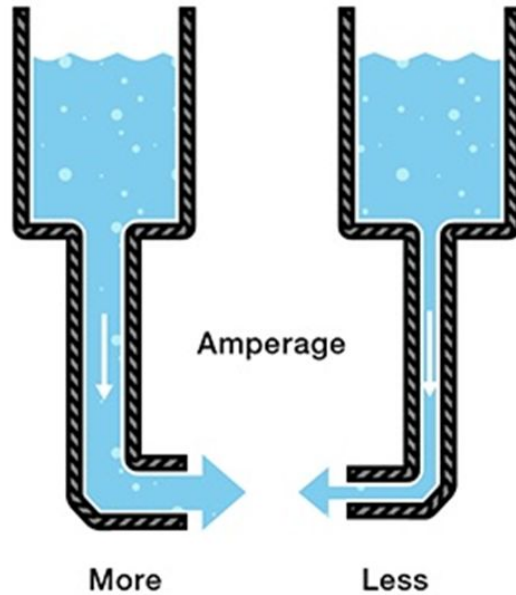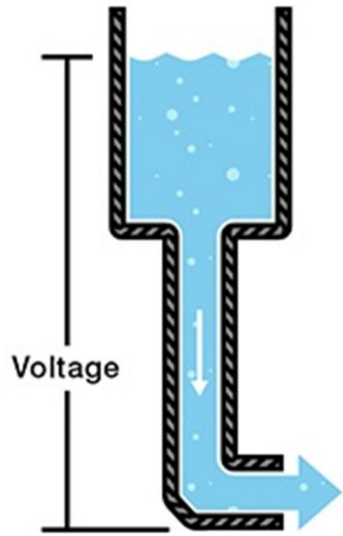
We can use the water analogy for voltage, current, and resistance



Ohm's Law relates these quantities

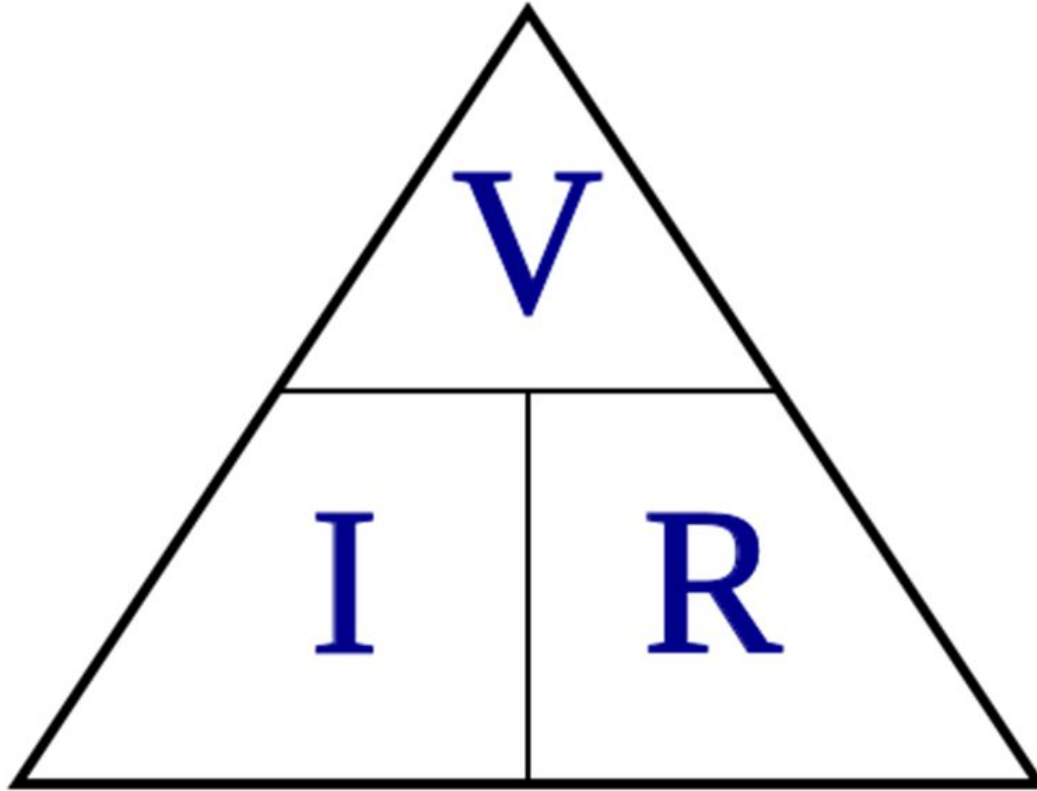

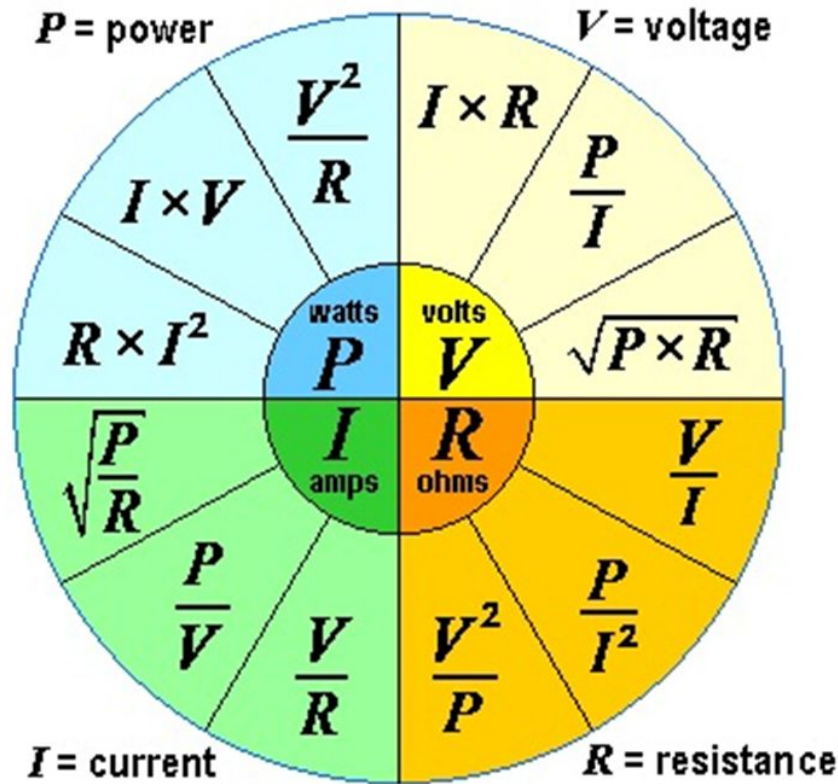Ohm's Law relates all of these quantities



There are common values, we recommend 1% or better










 


	Colour	Band 1 First digit	Band 2 Second digit	Band 3 Multiplier	Band 4 Tolerance
	Black	0	0	x 1 (x 1)	-
	Brown	1	1	x 10 (x 10)	1%
	Red	2	2	x 100 (x 100)	2%
	Orange	3	3	x 1 000 (x 1k)	not used
	Yellow	4	4	x 10 000 (x 10k)	not used
	Green	5	5	x 100 000 (x 100k)	not used
	Blue	6	6	x 1 000 000 (x 1M)	not used
	Violet	7	7	-	not used
	Grey	8	8	-	not used
	White	9	9	-	not used
	Gold	-	-	-	5%
	Silver	-	-	-	10%

Table J.1 Standard Resistance Values


5% Resistor Values (kΩ)	1% Resistor Values (kΩ)			
	100-174	178-309	316-549	562-976
10	100	178	316	562
11	102	182	324	576
12	105	187	332	590
13	107	191	340	604
15	110	196	348	619
16	113	200	357	634
18	115	205	365	649
20	118	210	374	665
22	121	215	383	681
24	124	221	392	698
27	127	226	402	715
30	130	232	412	732
33	133	237	422	750
36	137	243	432	768
39	140	249	442	787
43	143	255	453	806
47	147	261	464	825
51	150	267	475	845
56	154	274	487	866
62	158	280	499	887
68	162	287	511	909
75	165	294	523	931
82	169	301	536	953
91	174	309	549	976

Find the current flowing through the following circuit

Resistors in parallel and sum in different ways

Series Resistors

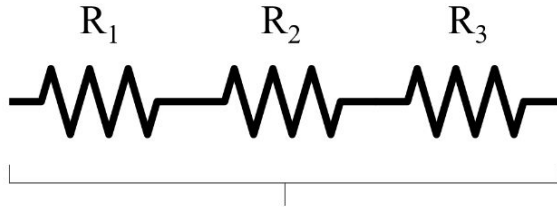
Current is the same across each resistor. Voltage is divided.



$$R_{Equivalent} = R_1 + R_2 + \dots + R_{N-1} + R_N$$

Parallel Resistors

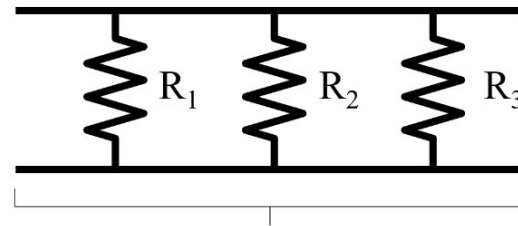
Voltage is the same across each resistor. Current is divided.



$$R_{Equivalent} = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2} + \dots + \frac{1}{R_{N-1}} + \frac{1}{R_N}}$$

Now, find the current limiting resistor required for this circuit

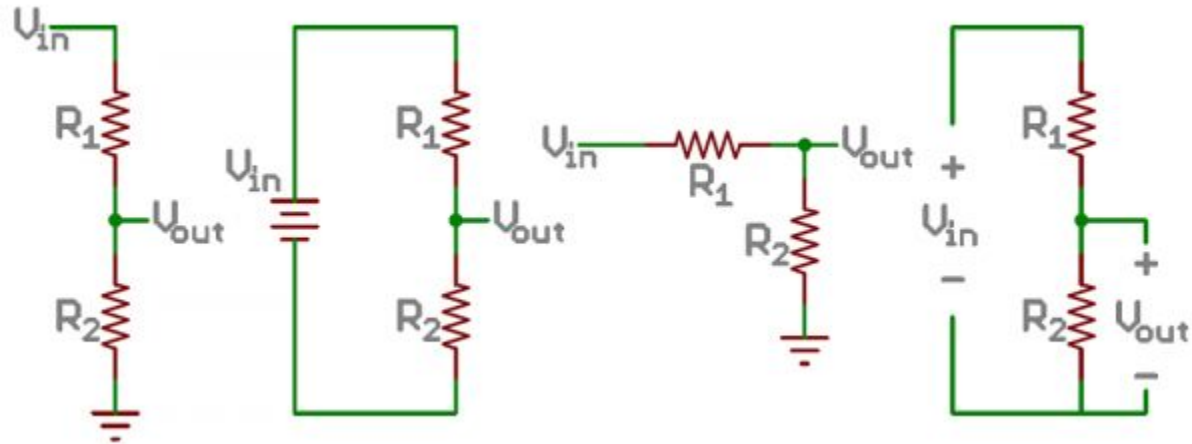Voltage dividers are a building block you'll find over and over



$$V_{out} = V_{in} \cdot \frac{R_2}{R_1 + R_2}$$

Wire - it is a component too!




Connectors




Common Circuits You May Encounter


Start/Stop Circuit

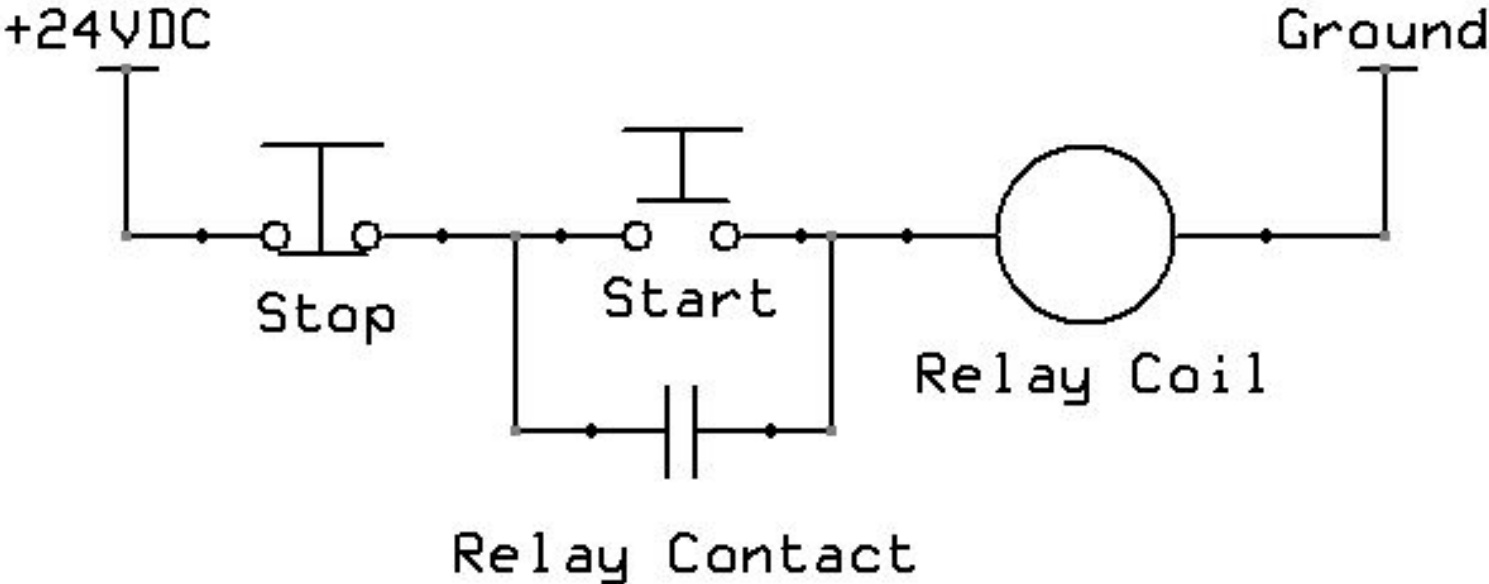

Failsafe Circuit

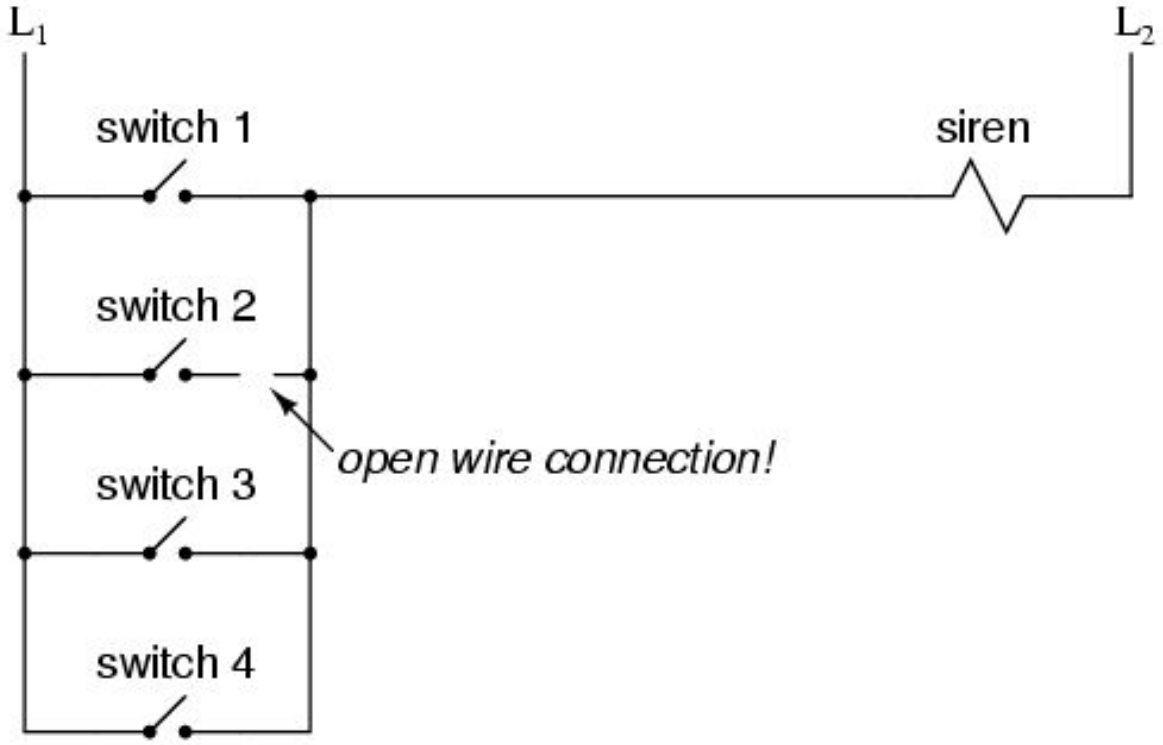

Failsafe Circuit

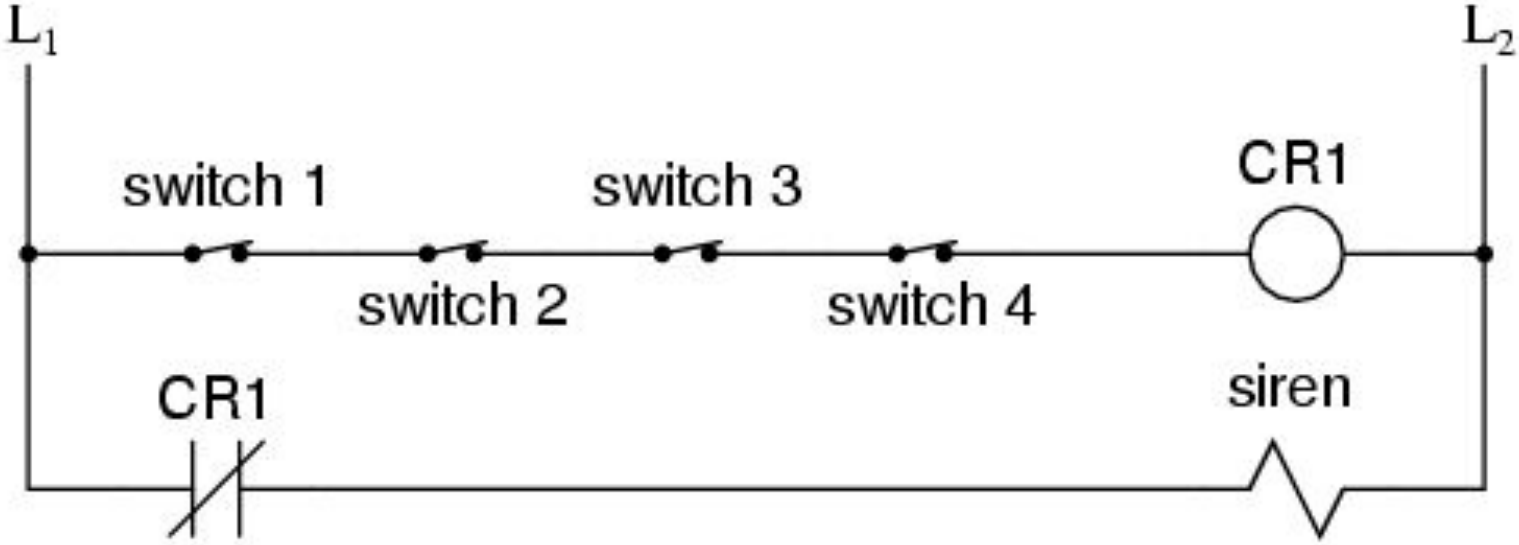

Common Equipment

